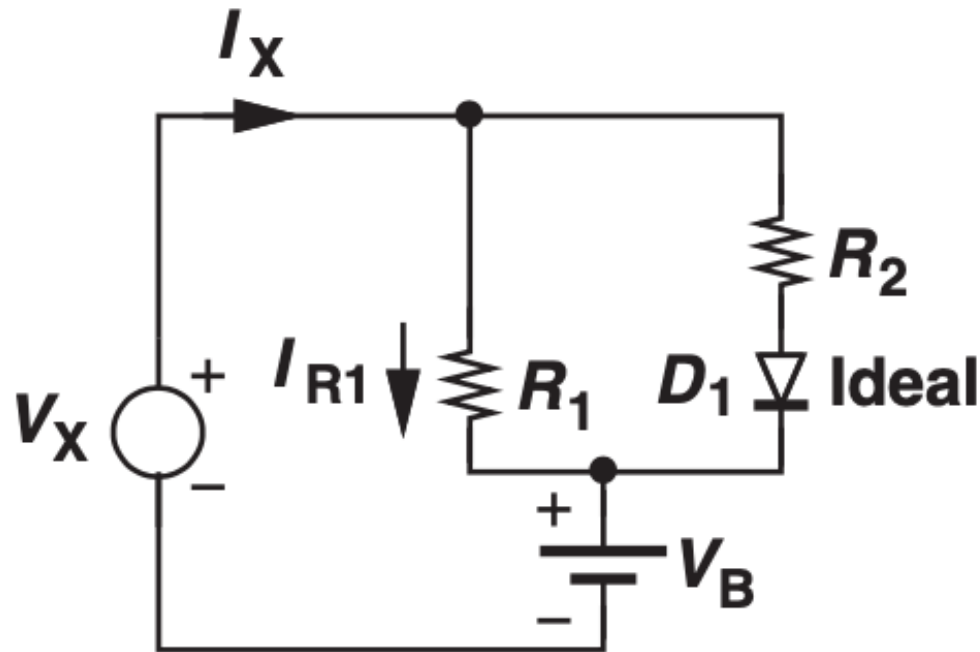


# Problem 1

- For the circuit depicted in Fig. below, plot  $I_X$  and  $I_{R1}$  as a function of  $V_X$  for two cases:  $V_B = -1V$  and  $V_B = +1V$ .



# Problem 1: solution




- $D_1$  is off  $\Rightarrow I_x = I_R = \frac{V_x - V_B}{R_1}$

- $D_1$  is on  $\Rightarrow I_x = \frac{V_x - V_B}{R_1 // R_2} = \frac{R_1 + R_2}{R_1 R_2} (V_x - V_B)$

- and  $I_R = \frac{I_x \times R_2}{R_1 + R_2} = \frac{V_x - V_B}{R_1}$


- Intersection of both equations occurs at  $V_x = V_B$

- For  $V_B = -1V$

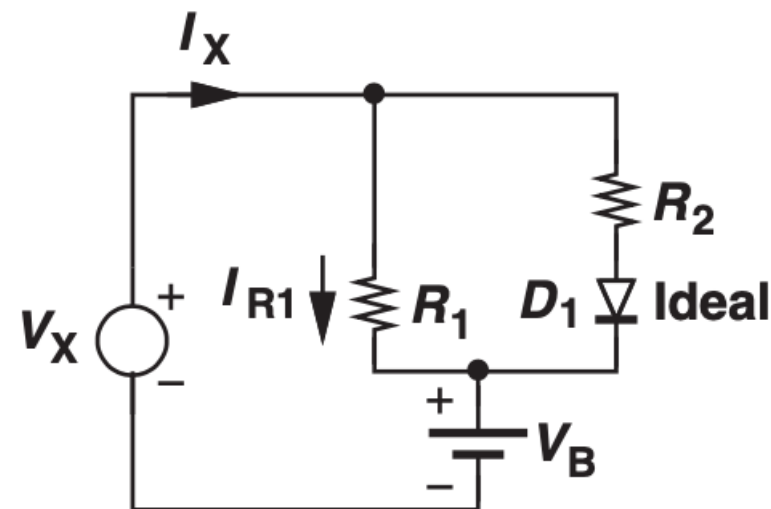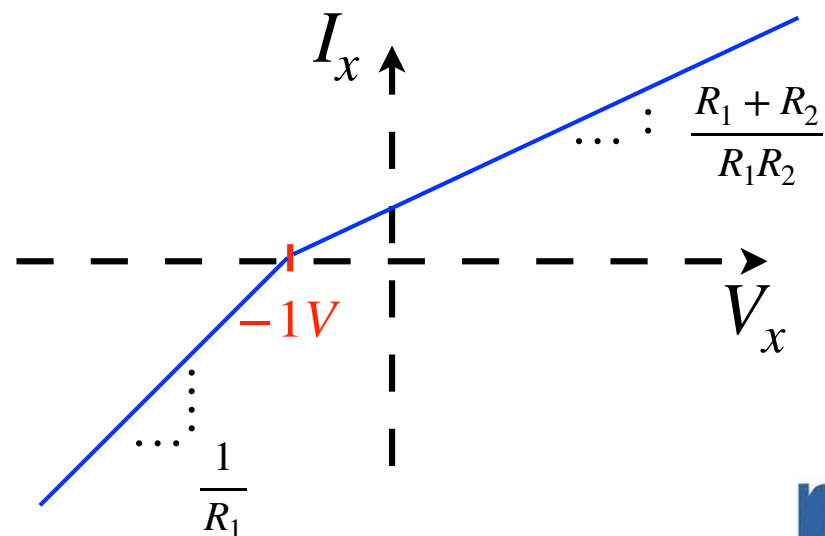
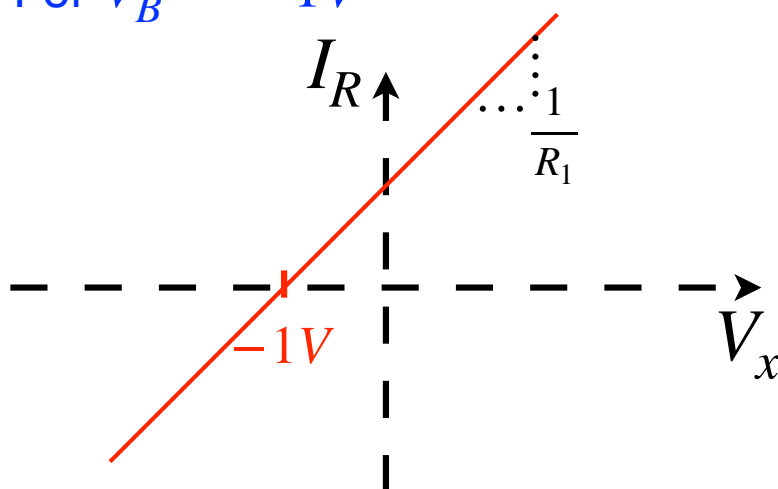

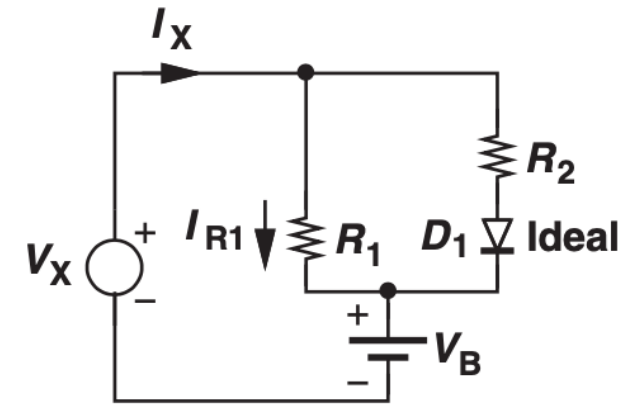
# Problem 1: solution

- $D_1$  is off  $\Rightarrow I_x = I_R = \frac{V_x - V_B}{R_1}$
- $D_1$  is on  $\Rightarrow I_x = \frac{V_x - V_B}{R_1 // R_2} = \frac{R_1 + R_2}{R_1 R_2} (V_x - V_B)$
- and  $I_R = \frac{V_x - V_B}{R_1}$




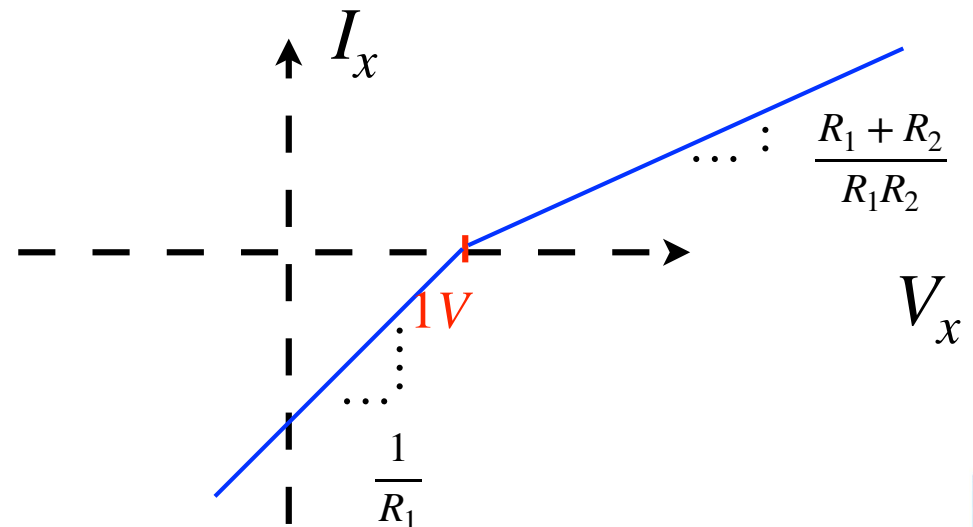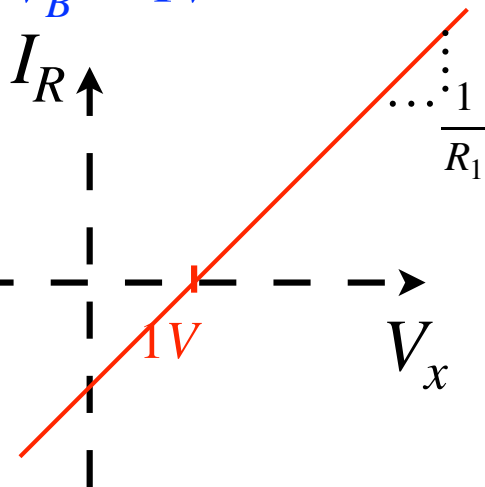- Intersection of both equations occurs at  $V_x = V_B$
- For  $V_B = 1V$


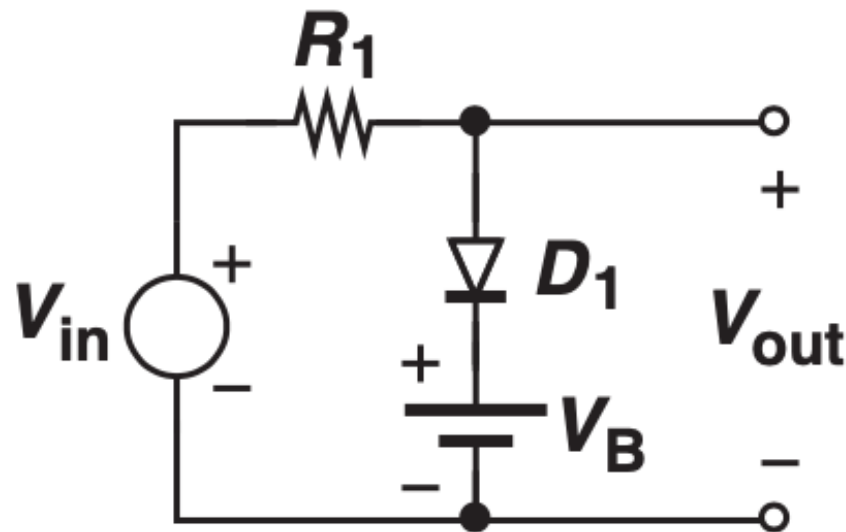
# Problem 2




- Plot the input/output characteristics of the circuits shown in Fig. below using an ideal model for the diodes.


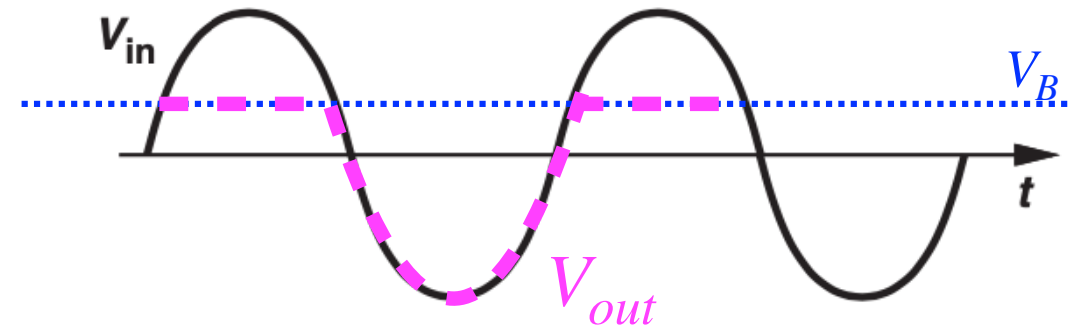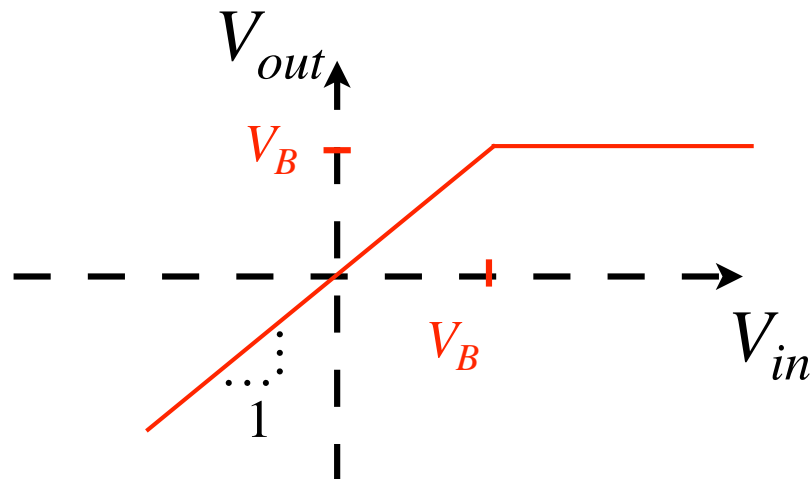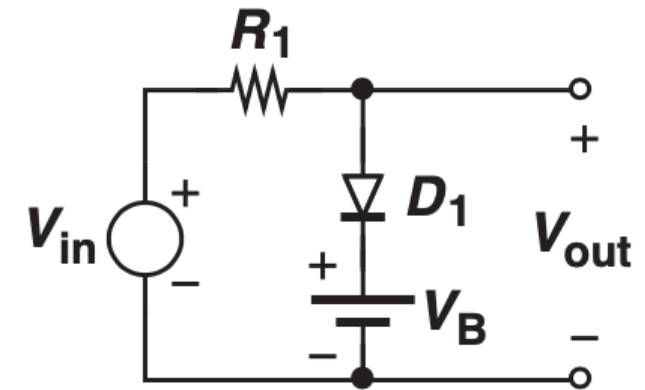
# Problem 2:solution


- $D_1$  is off  $\Rightarrow V_{out} = V_{in}$
- $D_1$  is on  $\Rightarrow V_{out} = V_B$
- intersection of both equations @  $V_{in} = V_B$

$$V_{out} = \begin{cases} V_{in} & \text{if } V_{in} < V_B \\ V_B & \text{if } V_{in} > V_B \end{cases}$$



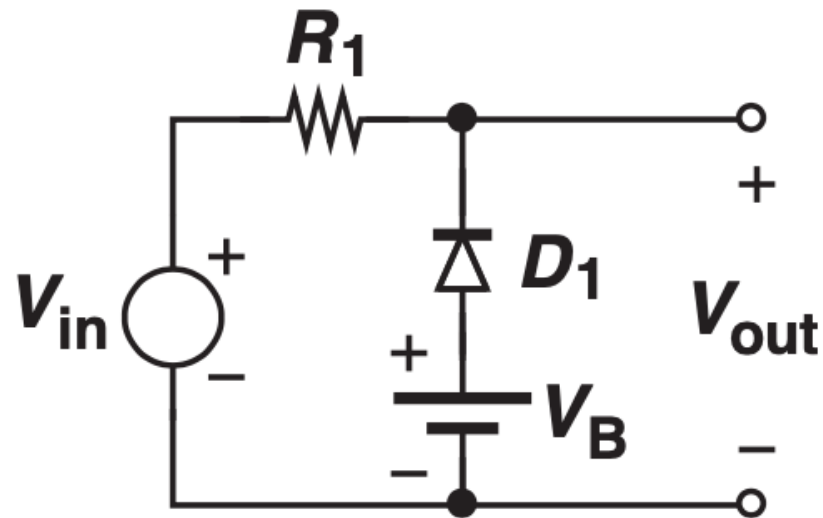
# Problem 3

- Plot the input/output characteristics of the circuits shown in Fig. below using constant-voltage model for the diodes.




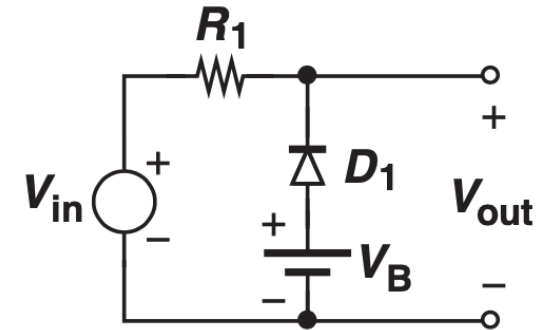
# Problem 3:solution

- $D_1$  is off  $\Rightarrow V_{out} = V_{in}$
- $D_1$  is on  $\Rightarrow V_{out} = V_B - V_{D,on}$
- intersection of both equations @  $V_{in} = V_B - V_{D,on}$



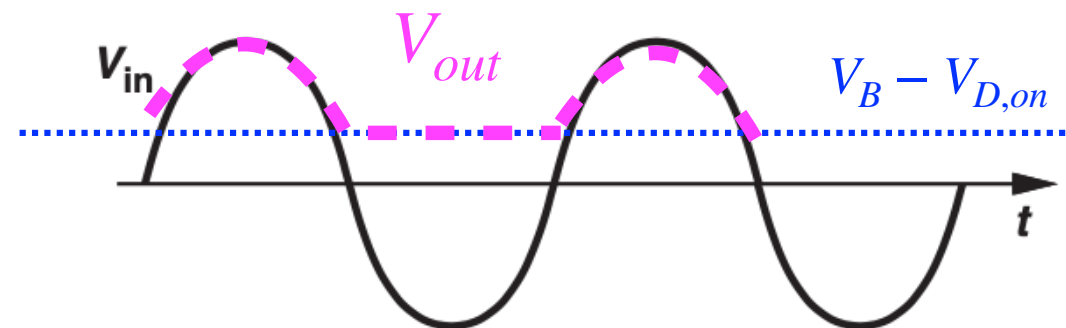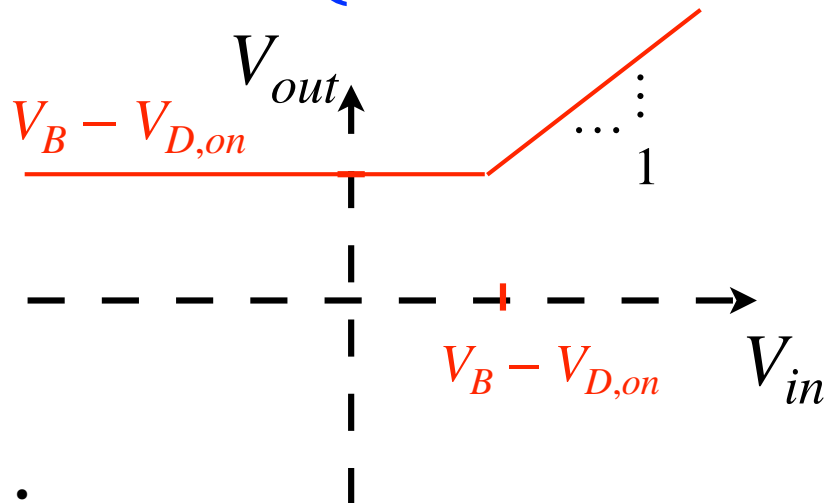
$$V_{out} = \begin{cases} V_{in} & \text{if } V_{in} > V_B - V_{D,on} \\ V_B - V_{D,on} & \text{if } V_{in} < V_B - V_{D,on} \end{cases}$$



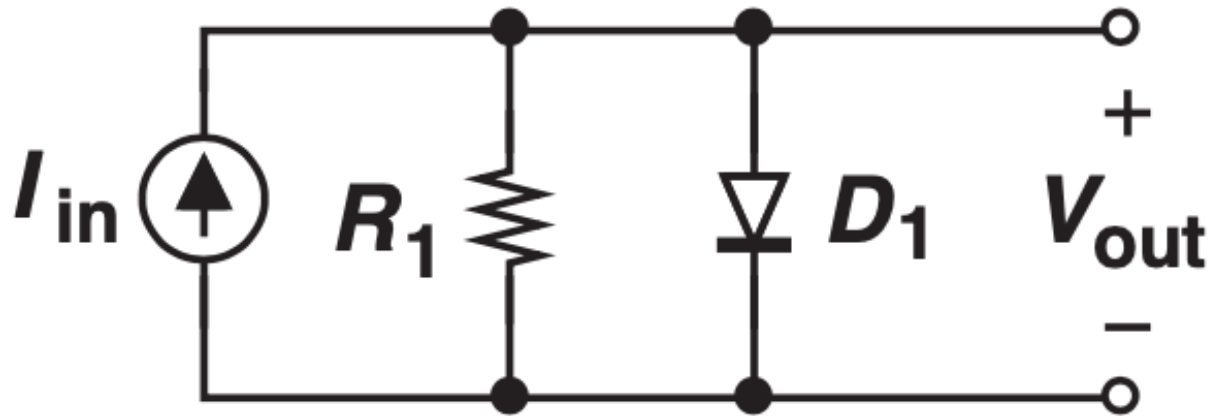
# Problem 4

- Plot  $V_{out}$  as a function of  $I_{in}$  for the circuit shown in figure below. Assume constant-voltage model.  $I_{in} = I_0 \cos(\omega t)$ .





# Problem 4:solution

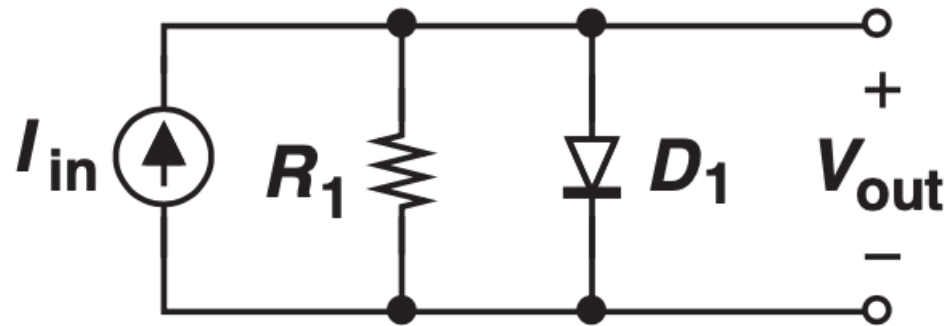


- $D_1$  is off  $\Rightarrow V_{out} = R_1 I_{in} = R_1 I_0 \cos(\omega t)$

- $D_1$  is on  $\Rightarrow V_{out} = V_{D,on}$


- Intersection @  $I_{in} = \frac{V_{D,on}}{R_1}$

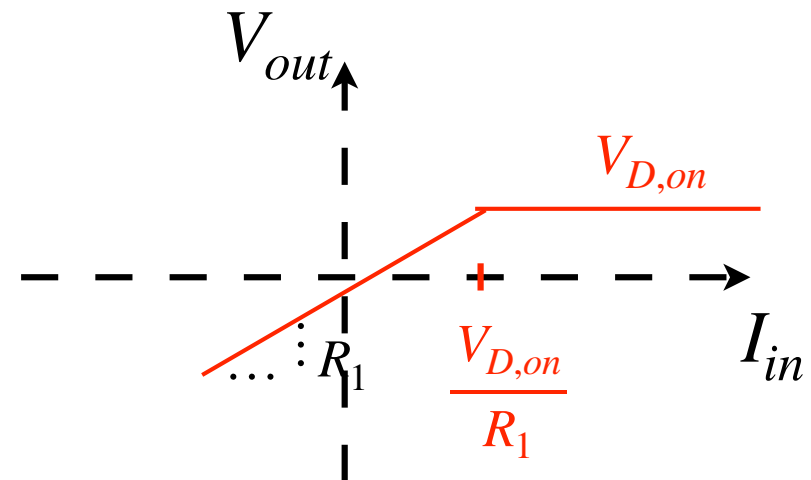- $$V_{out} = \begin{cases} R_1 I_{in} & \text{if } I_{in} < \frac{V_{D,on}}{R_1} \\ V_{D,on} & \text{if } I_{in} > \frac{V_{D,on}}{R_1} \end{cases}$$


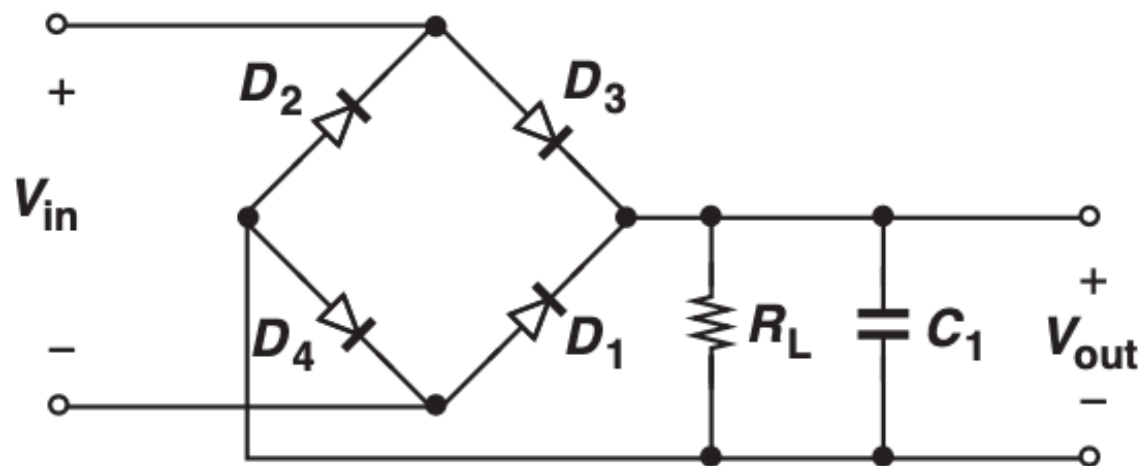
# problem 5

- A full-wave rectifier is driven by a sinusoidal input  $V_{in} = V_0 \cos \omega t$ , where  $V_0 = 3V$  and  $\omega = 2\pi$  (60 Hz). Assuming  $V_{D,on} = 800$  mV, determine the ripple amplitude with a  $1000\text{-}\mu\text{F}$  smoothing capacitor and a load resistance of  $30\ \Omega$ .



# problem 5: solution

- A full-wave rectifier is driven by a sinusoidal input  $V_{in} = V_0 \cos \omega t$ , where  $V_0 = 3V$  and  $\omega = 2\pi$  (60 Hz). Assuming  $V_{D,on} = 800$  mV, determine the ripple amplitude with a 1000- $\mu F$  smoothing capacitor and a load resistance of 30 .

- $$V_R = \frac{1}{2} \frac{V_0 - 2V_{D,on}}{R_L C f_{in}} = 0.389V$$

- If half-wave rectifier is used:

- $$V_R = \frac{V_0 - V_{D,on}}{R_L C f_{in}} = 2.55V$$