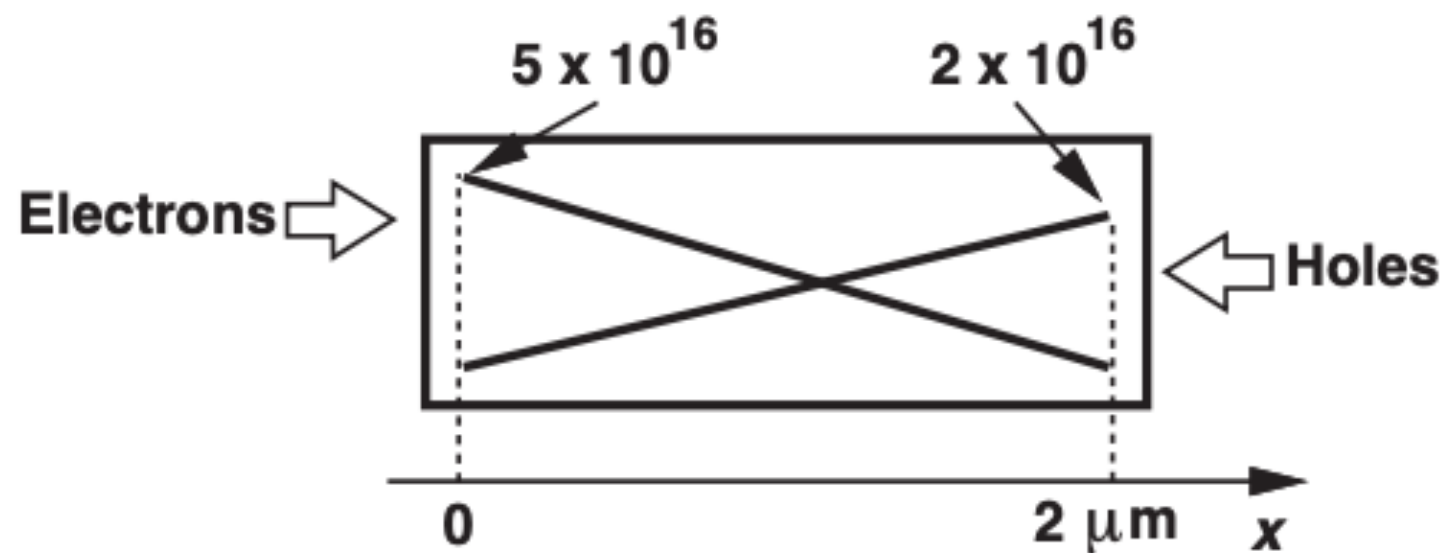


Problem 1


- Figure below shows a p -type bar of silicon that is subjected to electron injection from the left and hole injection from the right. Determine the total current flowing through the device if the cross section area is equal to $1\ \mu\text{m} \times 1\ \mu\text{m}$.

$$D_n = 34\text{cm}^2/\text{s} \quad D_p = 12\text{cm}^2/\text{s}$$



Problem 2

- Figure below shows two diodes with reverse saturation currents of I_{S1} and I_{S2} placed in series. Calculate I_B , V_{D1} , and V_{D2} in terms of V_B , I_{S1} , and I_{S2} .

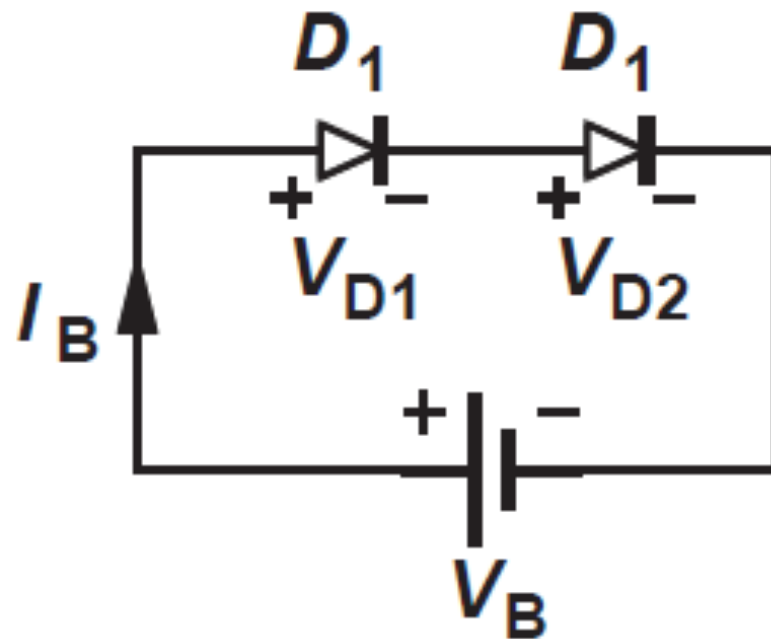

Problem 3

- In the circuit of Fig. below, we wish D_1 to carry a current of 0.5mA for $I_X = 1.3\text{mA}$. Determine the required reverse saturation current I_S .

